

Contents

Preface

xiii

Acknowledgements

xvii

1. Introduction to Electronics: Basic Ideas	1-18
1.1 Introduction	1
1.2 Atomic Structure: Bohr's Model	3
1.3 Bonding in Solid: Covalent Bonds	6
1.4 Energy Levels	8
1.5 Energy Band	9
1.6 Insulator, Conductor and Semiconductor	11
1.7 Conduction in Metals and Semiconductor	12
<i>Solved Numerical Problems</i>	15
<i>Multiple Choice Questions</i>	17
<i>Unsolved Problems</i>	17
2. Introduction to Semiconductor	19-73
2.1 Introduction to Solids and Crystals	19
2.2 Crystalline Solid	20
2.3 Crystal Systems and Bravais Lattices	21
2.4 Crystallographic Planes and Miller Indices	24
2.5 Coordination Number (N), Nearest Neighbour Distance (2r), Atomic Radius (r) and Packing Fraction (f)	27
2.6 Band Theory of Solids	31
2.7 Concept of Fermi Level	40
2.8 Fermi Levels in Different Materials: Metal, Semiconductor and Insulator	43
2.9 Classification of Semiconductors	44
2.10 Carrier Concentration in an Extrinsic Semiconductor	50
2.11 Degenerate and Non-Degenerate Semiconductor	52
2.12 E-K Diagram of Free Electrons	53
2.13 Direct and Indirect Band Gap Semiconductor	54
2.14 Effective Mass	56

2.15	Mobility	59
2.16	Transport Phenomena in Semiconductors	60
2.17	Electrical Conductivity of Semiconductors	62
	<i>Solved Numerical Problems</i>	64
	<i>Multiple Choice Questions</i>	67
	<i>Unsolved Problems</i>	71
3.	P-N Junction and P-N Junction Diode	74-210
3.1	P-N Junction	74
3.2	Analysis of a P-N Junction	76
3.3	P-N Junction under Biased Condition	90
3.4	P-N Junction diode: I-V Characteristics	93
3.5	Resistance of P-N Junction Diode	96
3.6	Equivalent Circuit	99
3.7	Diode Rectifiers	101
3.8	Figure of Merits of a Rectifier Circuit	109
3.9	Filter Circuits in Rectifiers	124
3.10	Breakdown Diodes: Avalanche and Zener Breakdown	140
3.11	Zener Diode as a Voltage Regulator	144
3.12	Clippers	149
3.13	Clamper Circuit	155
3.14	Voltage Multiplier Circuit	160
3.15	Special Purpose Diodes	162
	<i>Solved Numerical Problems</i>	169
	<i>Multiple Choice Questions</i>	191
	<i>Unsolved Problems</i>	199
4.	Bipolar Junction Transistor	211-261
4.1	Introduction	211
4.2	BJT: Construction and Terminals	211
4.3	Basic Operation and Action of a Transistor	213
4.4	Current Components in Transistor	219
4.5	Symbols of Transistor	225
4.6	Transistor Mode of Operation: CB, CE and CC Modes	226
4.7	Bipolar Junction Transistor as a Switch	235
4.8	Bipolar Junction Transistor as an Amplifier	237
4.9	Comparison of Different Modes of Operation	242
4.10	Transistor Limit of Operation	243
4.11	Thermal Runaway	244
	<i>Solved Numerical Problems</i>	244
	<i>Multiple Choice Questions</i>	254
	<i>Unsolved Problems</i>	259

5. Transistor Biasing and Stabilization	262-321
5.1 Introduction	262
5.2 Importance of Transistor Biasing	264
5.3 Transistor Biasing: Choosing the Operating Point	265
5.4 Load Line and Effect of Various Circuit Parameters on it	266
5.5 Importance of Optimum Choice of Q Point	274
5.6 AC Load Line	277
5.7 Stability Factors	280
5.8 Transistor Biasing Methods	281
5.9 Bias Compensation	295
<i>Solved Numerical Problems</i>	297
<i>Multiple Choice Questions</i>	311
<i>Unsolved Problems</i>	317
6. Modelling of BJT and Design of Amplifiers	322-406
6.1 Introduction	322
6.2 Small-Signal Analysis of BJT	323
6.3 Complete Small-Signal Equivalent Circuit of an Amplifier	345
6.4 Basic Transistor Amplifier Configurations	346
6.5 CE, CB and CC Amplifiers: Summary and Comparison	368
<i>Solved Numerical Problems</i>	368
<i>Multiple Choice Questions</i>	397
<i>Unsolved Problems</i>	402
7. Field-Effect Transistors	407-475
7.1 Introduction	407
7.2 Construction and Symbolic Representation of JFET	409
7.3 Principles of Operation of JFET	411
7.4 Characteristics of JFET	416
7.5 Important Relationships: BJT and FET	420
7.6 JFET Parameter	421
7.7 Comparison between JFET and BJT	422
7.8 Biasing of JFET	423
7.9 JFET Amplifier	430
7.10 Introduction to MOSFET	437
<i>Solved Numerical Problems</i>	448
<i>Multiple Choice Questions</i>	466
<i>Unsolved Problems</i>	470
8. Feedback Amplifiers	476-519
8.1 Introduction	476
8.2 Basic Concept of Feedback	477
8.3 Effects of Feedback on Amplifier Characteristics	480
8.4 Analysis of Feedback Amplifiers	501

	<i>Solved Numerical Problems</i>	510
	<i>Multiple Choice Questions</i>	514
	<i>Unsolved Problems</i>	517
9.	Oscillators and Multivibrators	520-553
9.1	Introduction	520
9.2	Classification of Oscillators	521
9.3	Principle of Operation of Oscillator	522
9.4	Applications of Oscillators	524
9.5	Practical Oscillator Circuits	524
9.6	Multivibrators	538
	<i>Solved Numerical Problems</i>	544
	<i>Multiple Choice Questions</i>	549
	<i>Unsolved Problems</i>	551
10.	Power Amplifiers	554-589
10.1	Introduction	554
10.2	Performance Characteristics of Power Amplifiers	554
10.3	Classification of Power Amplifier	555
10.4	Class A Amplifier	558
10.5	Class B Amplifier	564
10.6	Class AB Amplifier	571
10.7	Class C Operation	572
10.8	Distortion in Amplifier	573
	<i>Solved Numerical Problems</i>	577
	<i>Multiple Choice Questions</i>	588
	<i>Unsolved Problems</i>	589
11.	Silicon Controlled Rectifiers	590-609
11.1	Introduction to Thyristor	590
11.2	Construction: Realization Using Transistors	591
11.3	Principle of Operation and Static Characteristic Curve	593
11.4	SCR ON - OFF Procedure (Triggering)	594
11.5	Application of SCR	595
11.6	Light-Activated SCR	599
11.7	DIAC	600
11.8	TRIAC	601
11.9	UJT	603
	<i>Solved Numerical Problems</i>	604
	<i>Multiple Choice Questions</i>	606
	<i>Unsolved Problems</i>	609
12.	Integrated Circuits	610-619
12.1	Introduction	610
12.2	IC: Advantages and Disadvantages	611

12.3	IC Classification	612
12.4	IC Fabrication Process	615
	<i>Multiple Choice Questions</i>	618
13.	Operational Amplifier	620-709
13.1	Introduction	620
13.2	Historical Perspective	622
13.3	The Ideal OPAMP Model	623
13.4	Deviation from Ideal OPAMP	624
13.5	Open-loop Operation	625
13.6	Some Important Parameters of OPAMP	627
13.7	Block Diagram Representation of Different Stages of OPAMP	631
13.8	Applications of OPAMP	632
	<i>Solved Numerical Problems</i>	668
	<i>Multiple Choice Questions</i>	694
	<i>Unsolved Problems</i>	698
	<i>Exercise</i>	706
14.	Analog Communication	710-750
14.1	Introduction	710
14.2	Elements of Communication System	711
14.3	Classification of Communication System	713
14.4	Classification Based on Media	715
14.5	Classification Based on Technology	723
	<i>Solved Numerical Problems</i>	742
	<i>Multiple Choice Questions</i>	745
	<i>Exercise</i>	750
15.	Introduction to Digital Logic Circuits	751-810
15.1	Introduction	751
15.2	Different Number Systems	752
15.3	Two Common Binary Codes: BCD and Gray Code Format	756
15.4	Conversion from One Number System to Another	757
15.5	Binary Arithmetic	760
15.6	Logic Circuits	769
15.7	De Morgan's Theorem	776
15.8	Universal Logic Gate	776
15.9	Circuit Realization of Logic Gates	778
15.10	Boolean Algebra and Simplification of Logic Functions	780
15.11	Two Different Forms of Boolean Expression	783
15.12	Classification of Digital Circuits	785
	<i>Solved Numerical Problems</i>	802
	<i>Multiple Choice Questions</i>	807
	<i>Exercise</i>	809